



# **DIGITAL ELECTRONICS**

**By:**

**NEETI**

**Lecturer (ECE)**



# COUNTERS

# COUNTER



A counter is a sequential circuit consisting of a combination of flip-flops used for counting the pulses.

Depending upon the manner in which flip-flops of the counter are triggered, there are two types of counters:


1. **Asynchronous counter:** If the flip-flops of a counter do not change their state at the same instant, then such counters are called asynchronous counters.

2. **Synchronous counters:** In the synchronous counter, clock input is given to all the flip-flops of the counter. So, in the synchronous counter, all flip-flops change their state at the same instant, that is why such type of counter is called synchronous counter.

# 2-BIT ASYNCHRONOUS COUNTER

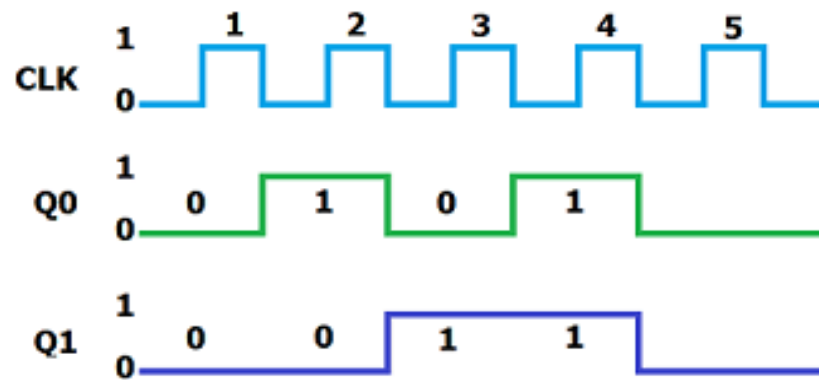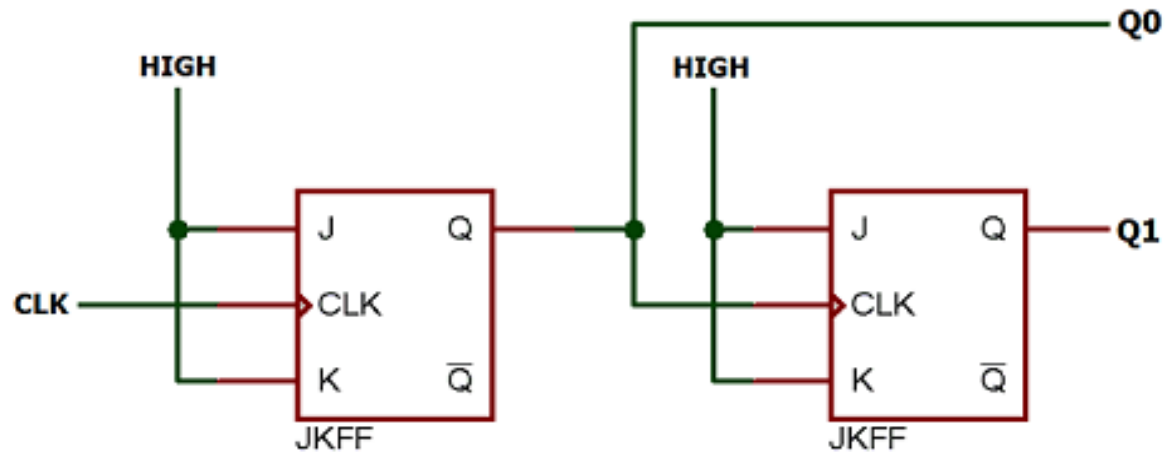

# 4-BIT ASYNCHRONOUS COUNTER

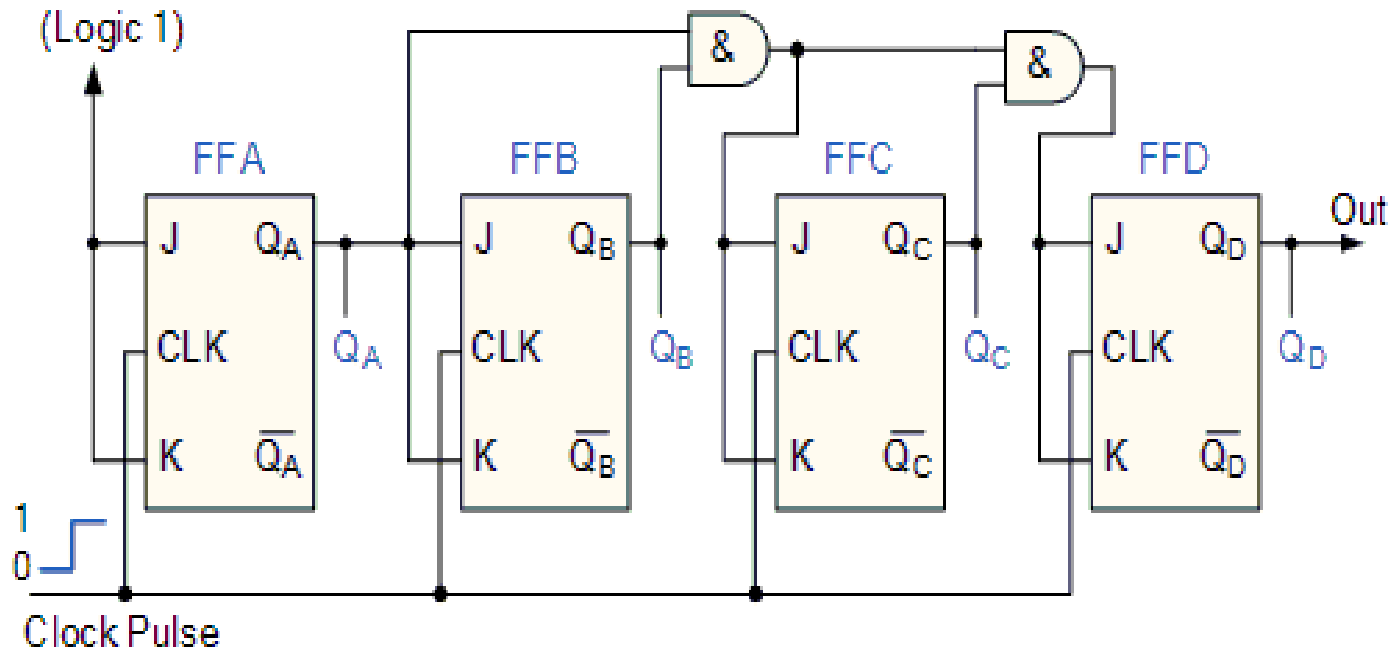


# MODULUS COUNTER


- The **modulus** (or just **modulo**) is the number of states the **counter** counts and is the dividing number of the **counter**. **Modulus Counters**, or simply **MOD counters**, are defined based on the number of states that the **counter** will sequence through before returning back to its original value.
- A MOD-N counter can be used to divide the input clock frequency by N as the frequency of the output of last flip-flop will be one by-N of the input clock frequency. So a MOD-N counter is also called Divide by N counter.
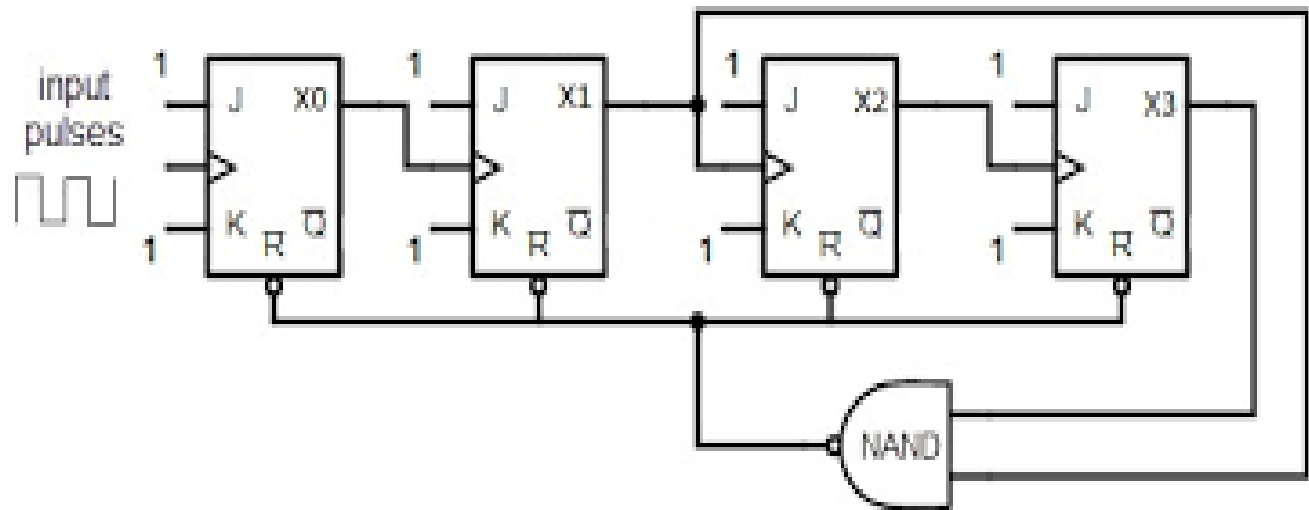
# DECADE COUNTER

- A **decade counter** is one that counts in decimal digits, rather than binary. It counts from 0 to 9 and then resets to zero. The **counter** output can be set to zero by pulsing the reset line low. The **count** then increments on each clock pulse until it reaches 1001 (decimal 9).



# 3 BIT SYNCHRONOUS COUNTER

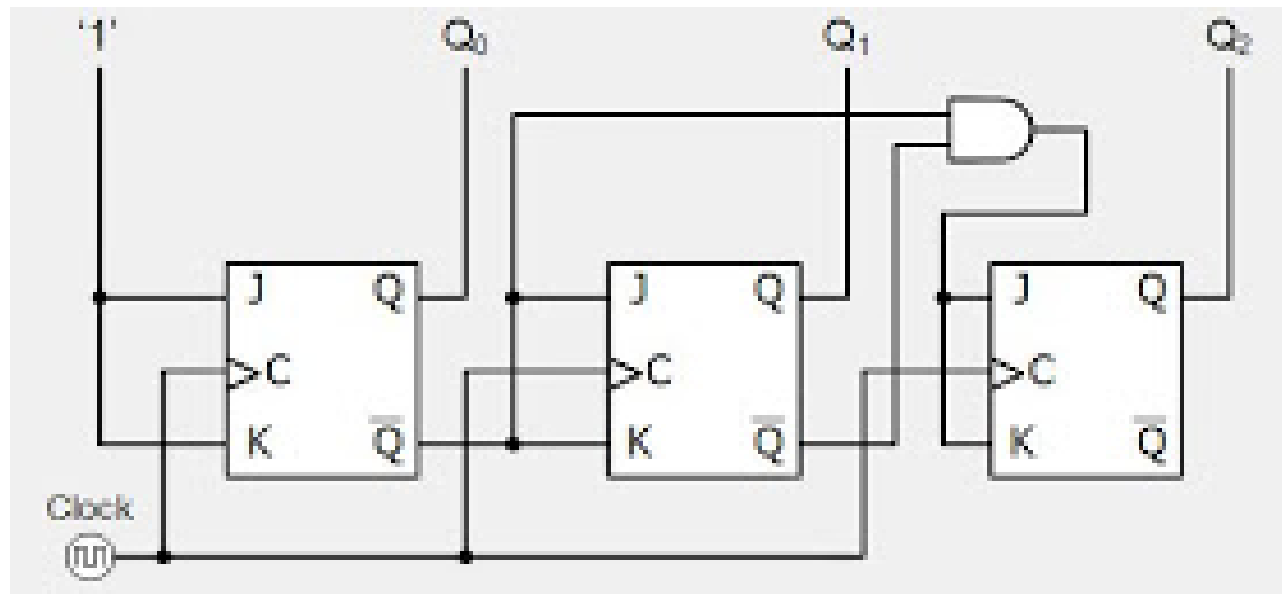

# APPLICATIONS OF COUNTERS

- Frequency **counters**.
- Digital clocks.
- Analog to digital convertors.
- With some changes in their design, **counters** can be used as frequency divider circuits.
- In time measurement.
- We can design digital triangular wave generator by using **counters**.



# **SHIFT REGISTERS**

# SHIFT REGISTER

- Shift register is a combination of flip-flops and primarily used to store the data and shifting the data in a digital system..
- It has no specified sequence of states.
- Data are entered in the form of 0 and 1 by some external source.
- The shifting capability of shift register means the movement of data from one flip-flop to next flip-flop with the application of clock input.


# TYPES OF SHIFT REGISTER

Depending upon the manner by mean of which data are loaded or data are retrieved , there are four types of shift register:

1. Serial in serial out shift register.
2. Serial in parallel out shift register.
3. Parallel in serial out shift register.
4. Parallel in parallel out shift register.

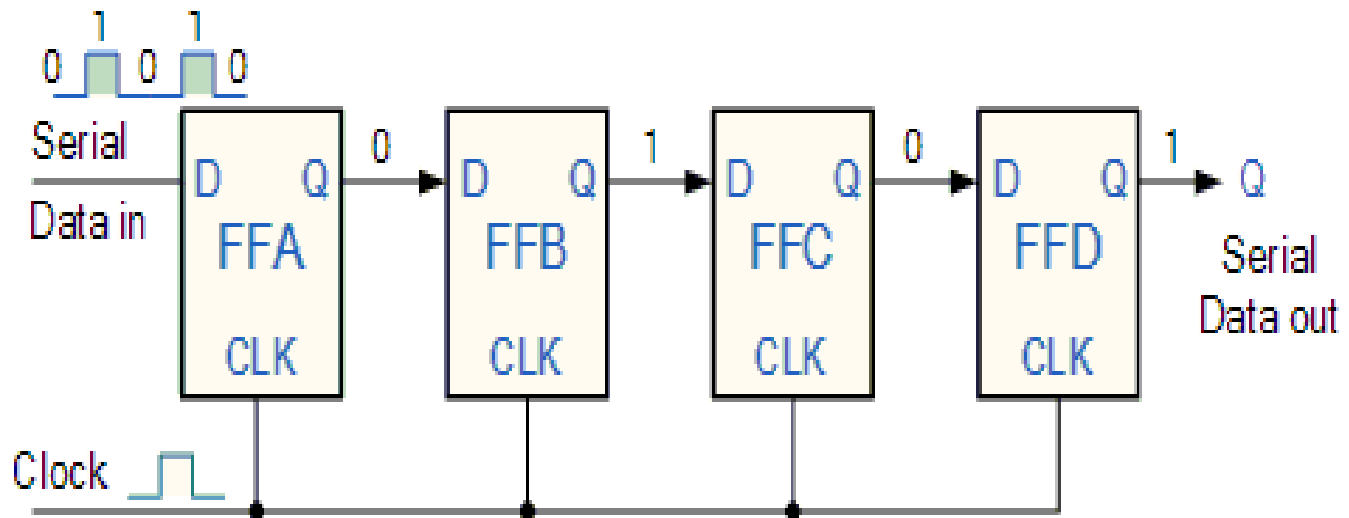
# SERIAL IN SERIAL OUT SHIFT REGISTER

- **Serial In Serial Out (SISO) shift** registers are a kind of **shift** registers where both data loading as well as data retrieval to/from the **shift register** occurs in **serial**-mode.



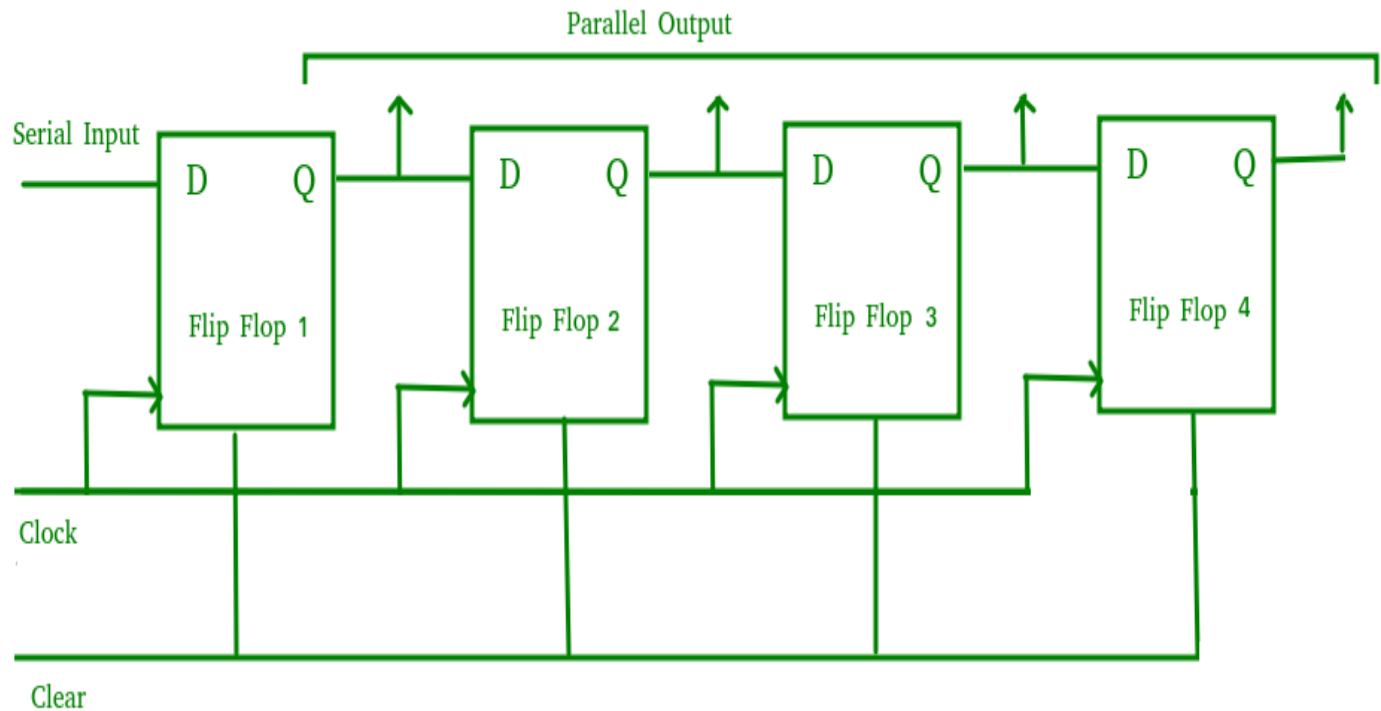
# SERIAL IN PARALLEL OUT SHIFT REGISTER

- In **Serial In Parallel Out (SIPO) shift** registers, the data is stored into the register serially while it is retrieved from it in **parallel**-fashion.


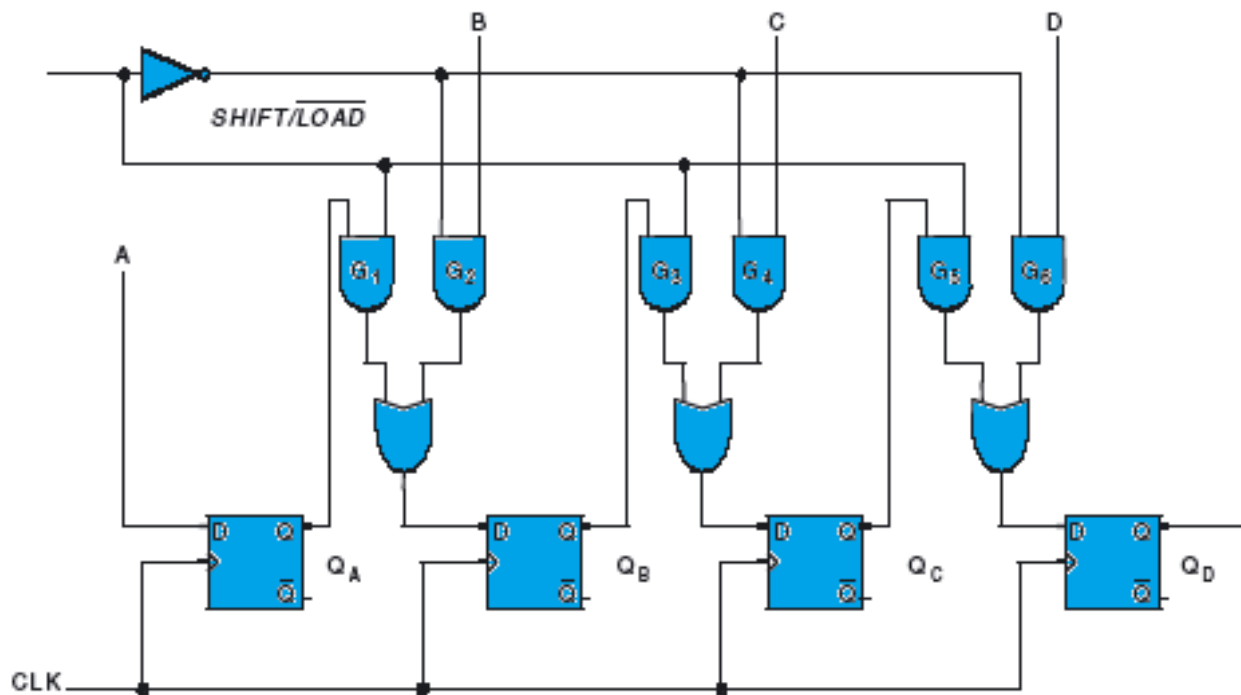
# PARALLEL IN SERIAL OUT SHIFT REGISTER


In **Parallel In Serial Out (PISO)** shift registers, the data is loaded onto the **register** in **parallel** format while it is retrieved from it serially.



A 4-bit parallel-in-serial-out shift register.
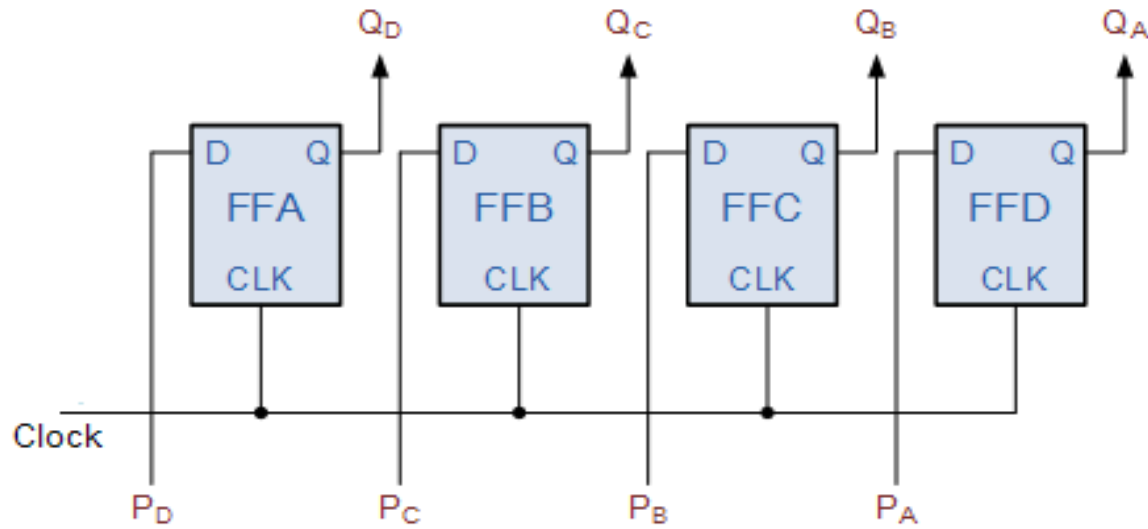
# PARALLEL IN PARALLEL OUT SHIFT REGISTER

**Parallel In Parallel Out (PIPO)** shift registers are the type of storage devices in which both data loading as well as data retrieval processes occur in parallel mode.






# **ANALOG TO DIGITAL AND DIGITAL TO ANALOG CONVERTOR**

# DIGITAL TO ANALOG CONVERTOR

- The device which converts digital quantity to analog quantity is known as digital to analog (D/A) convertor.
- In most of the electronics equipment, processing of the signal is done in digital form and after processing, these signals are converted in analog form.
- There are two different types of D/A convertor:
  1. Binary weighted D/A convertor
  2. R/2R ladder D/A convertor.

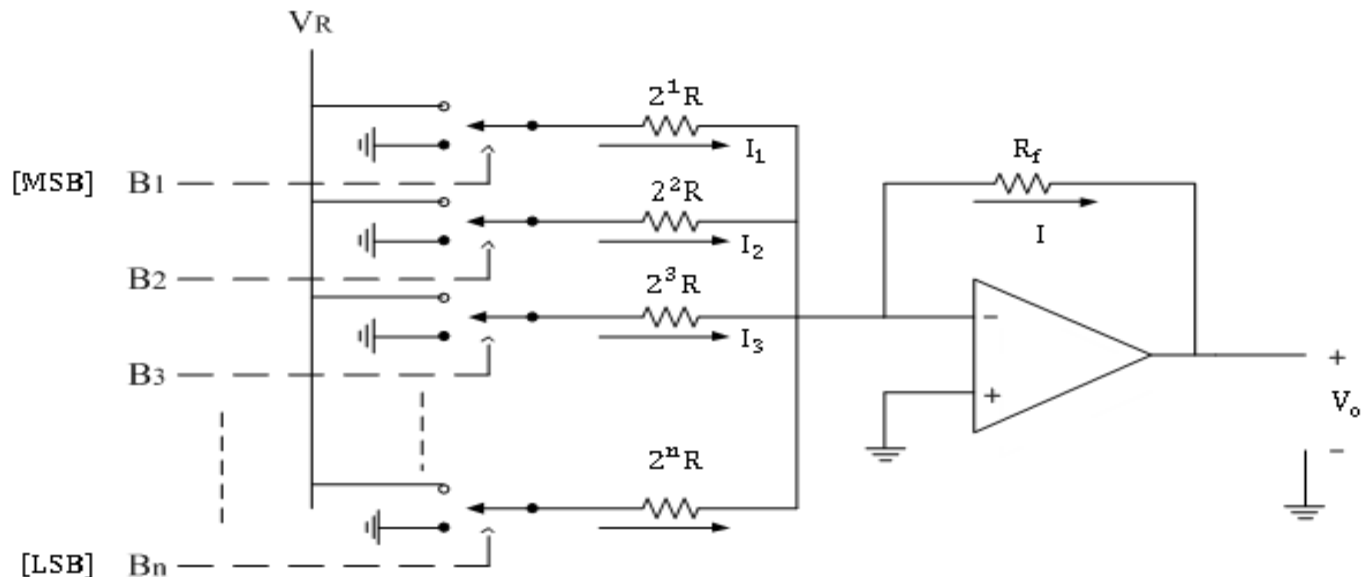
# BINARY WEIGHTED D/A CONVERTOR

This D/A convertor involve a resistive network and an operational amplifier. Each resistor of the network represent the binary weight of the input bits of the digital code. The operational amplifier provides a very high input impedance and connected in inverting mode.


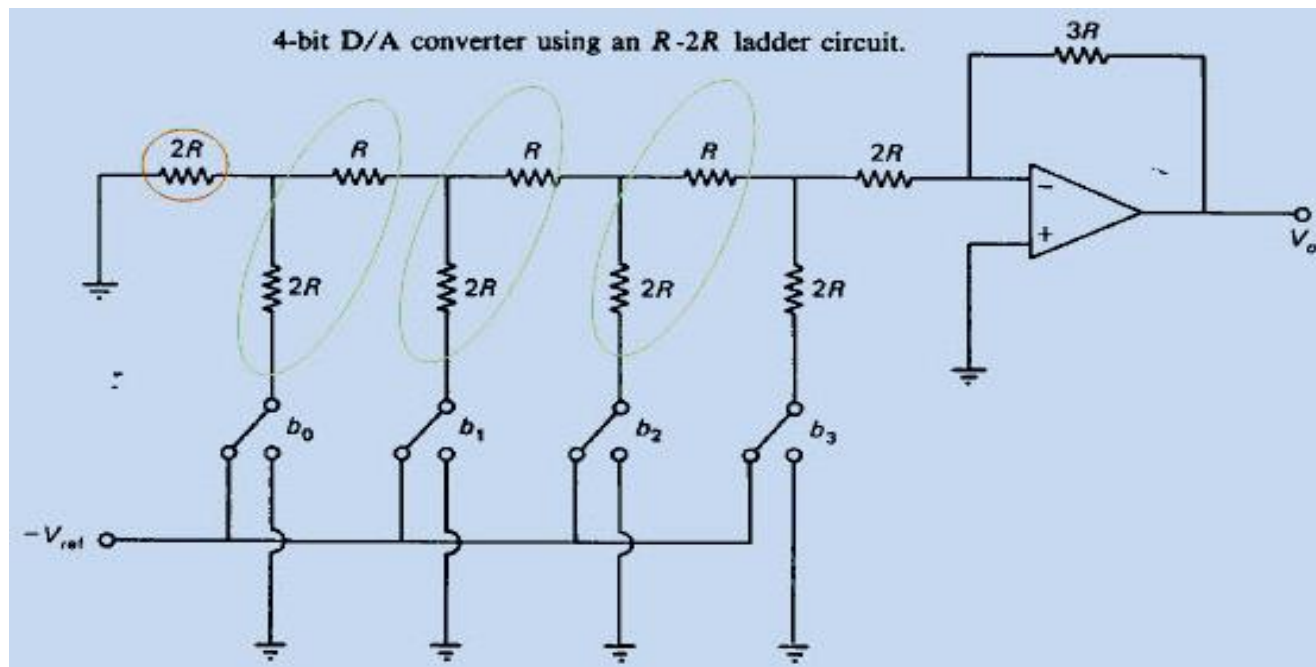
# R/2R LADDER D/A CONVERTOR

This type of D/A convertor involve only two resistor values,  $R$  and  $2R$  for any number of data input bits. So the problem of wide range of resistor value in case of binary weighted D/A is overcome in this type of D/A convertor.




# ANALOG TO DIGITAL CONVERTOR

In the analog to digital (A/D) convertor, the analog quantity is converted in to digital form. There are different types of analog to digital convertor:

1. Flash A/D convertor
2. Stair step ramp A/D convertor
3. Single slope A/D convertor
4. Dual slope A/D convertor
5. Successive approximation A/D convertor
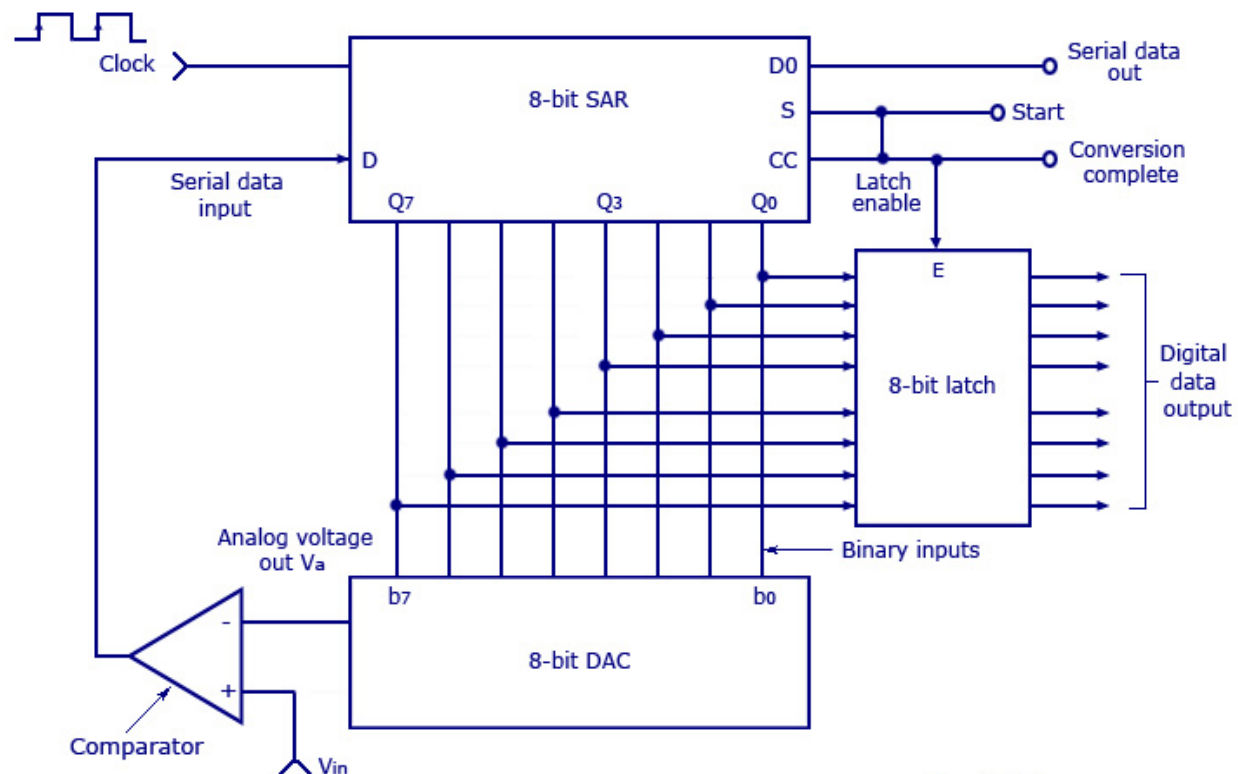
# SUCCESSIVE APPROXIMATION A/D CONVERTOR

A successive approximation A/D converter consists of a comparator, a successive approximation register (SAR), output latches, and a D/A converter.



# DUAL SLOPE A/D CONVERTOR

In **dual slope** type **ADC**, the integrator generates two different ramps, one with the known analog input voltage  $V_A$  and another with a known reference voltage  $-V_{ref}$ . Hence it is called a **dual slope** A to D converter.

